

Resonance Quick Sheet

Print Last Name giftakis Print First Name ben

Section _____ Date _____ TA _____

(1) **Values:**

$$C_1 (\mu\text{F}) = \underline{.1001} \quad C_2 (\mu\text{F}) = \underline{.097}$$

(2) Measurement with one capacitor.

$$C_1 (\text{F}) = \underline{1.001\text{E-}7 \text{ F}} \text{ Enter your result in scientific notation.}$$

$$f_0 = \underline{2000 \text{ hz}} \text{ Enter your result to 4 digits.}$$

(3) Measurement with capacitors in series.

$$C_{\text{series}} (\text{F}) = \underline{4.93\text{E-}08 \text{ F}} \text{ Enter your result in scientific notation.}$$

$$f_0 = \underline{2900\text{hz}} \text{ Enter your result to 4 digits.}$$

(4) Measurement with capacitors in parallel.

$$C_{\text{parallel}} (\text{F}) = \underline{1.97\text{E-}7 \text{ F}} \text{ Enter your result in scientific notation.}$$

$$f_0 = \underline{1400\text{hz}} \text{ Enter your result to 4 digits.}$$

(5) Results.

$$L_{\text{exp}} (\text{mH}) = \underline{56.98}$$

$$\% \text{ difference} = \underline{9.55\%}$$