

Kirchhoff's Law Quick Sheet

Print Last Name giftakis Print First Name ben

Section _____ Date _____ TA _____

Lab Partner _____

(1) **Individual Resistors Measured (34405A)** $R_1 = \underline{.005 \text{ kilohms}}$ $R_2 = \underline{.01 \text{ kilohms}}$ $R_3 = \underline{.015 \text{ kilohms}}$

(2) **Parallel Combination Measured (34405A)** **Experimental:** $R_p = \underline{.00272 \text{ kilohms}}$

Theoretical: $R_p = [1/R_1 + 1/R_2 + 1/R_3]^{-1} = \underline{0.00273 \text{ kilohms}}$ (use measured values of R)

Series Combination Measured (34405A) **Experimental:** $R_s = \underline{.03 \text{ kilohms}}$

Theoretical: $R_s = R_1 + R_2 + R_3 = \underline{.03 \text{ kilohms}}$ (use measured values of R)

(3) **Study of Simple Circuits: Kirchhoff's Voltage Law**

Applied Voltage $V_{emf} = \underline{10V}$ (Ten Volts) **Part 3B Experimental:** $I = \underline{330mA}$

Measured (Agilent 34405A)

All values should be positive.

$$V_1 = \underline{1.67 \text{ V}}$$

$$V_2 = \underline{3.33 \text{ V}}$$

$$V_3 = \underline{5 \text{ V}}$$

Predicted $V = IR$ (Use I Experimental & R Measured)

All values should be positive.

$$V_1 = \underline{1.65 \text{ V}}$$

$$V_2 = \underline{3.3 \text{ V}}$$

$$V_3 = \underline{4.95 \text{ V}}$$

Verification of Kirchhoff's Law $V_{emf} = V_1 + V_2 + V_3$

Using Measured values: $V_{emf} = \underline{10V}$ Using Predicted values: $V_{emf} = \underline{10V}$

(4) **Study of Simple Circuits: Kirchhoff's Current Law**

Applied Voltage = _____ (Five Volts)

Individual Measured Voltages and Currents. The node will be the low potential for measurements.

(Measured results will be both positive and negative.)

$$I_1 = \underline{\hspace{2cm}} \quad V_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}} \quad V_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}} \quad V_3 = \underline{\hspace{2cm}}$$

Predicted Currents (Use voltages measured in **Part (4)**, and the above **Part (1)** resistor measurements.)

$$I_1^* = \underline{\hspace{2cm}} \quad I_2^* = \underline{\hspace{2cm}} \quad I_3^* = \underline{\hspace{2cm}}$$

Verification of Kirchhoff's Current Law $I_1 + I_2 + I_3 = 0$

Using Measured values from Part 4B: $I_1 + I_2 + I_3 = \underline{\hspace{2cm}}$

Using Predicted Values from Part 4C: $I_1^* + I_2^* + I_3^* = \underline{\hspace{2cm}}$