

Voltage Divider Quick Sheet

Print Last Name _____ Print First Name _____

Section _____ Date _____ TA _____

Lab Partner _____

Measured Voltages for **Part 1.**

$V_{in} =$ _____

Slope from Excel graph and calculated value of pencil resistance

Slope = _____ $R_2 \pm S_{R2} =$ _____ % error = _____

Measured Voltages for **Part 2.**

Voltage drop across R_2 and wire. $V_{in} =$ _____

Voltage drop across wire. $V_{wire} =$ _____

Calculated $V_2 =$ _____ $V_2 = V_{in} - V_{wire}$

Calculate Current I in the circuit using V_2 and R_2 . Use R_2 measured from part (1) above.

$I =$ _____

Diameter D and Cross-sectional area A of the wire.

$D = 0.63 \text{ mm}$ $A =$ _____

Slope from Excel graph and calculated resistivity of the wire

Slope = _____ $\rho \pm S_\rho =$ _____ (This should be a positive number.)

Percent error to the accepted value of $\rho = 1.08 \mu\Omega\text{m}$.

% error = _____

Resistance of wire using Ohm's Law ($R_{3, \text{wire, Ohm}} = V_{\text{wire}}/I$).

$R_{3, \text{wire, Ohm}} =$ _____

Calculated value of resistance of the wire, $R_{3, \text{wire}}$, using length $L = 1.00$ meter, and the above values of A and ρ (parts 6 and 7). Calculate the percent error using the above measured value of $R_{3, \text{wire, Ohm}}$ as the accepted value.

Calculated $R_{3, \text{wire, } \rho} =$ _____ % error = _____