

Capacitor Series and Parallel Quick Sheet

Print Last Name giftakis Print First Name Benjamin

Section _____ Date _____ TA _____

Lab Partner _____

- (1) **Measured values** of R_1 , C_1 and C_2 . C_1 is already connected to R_1 . Use the $1\mu\text{F}$ range on the multimeter when measuring capacitance.

$$R_1 = \underline{34.96 \text{ kilohms}} \quad R_g = \underline{.05 \text{ kilohms}} \quad R = R_1 + R_g = \underline{35.01 \text{ kilohms}}$$

$$C_1 = \underline{.104 \text{ uF}} \quad C_2 = \underline{.099 \text{ uF}} \quad (\text{Three numbers after the decimal point.})$$

- (2) Using the slope from Excel and equation 9, calculate the capacitance of the first capacitor C_1 . Calculate the % error, where the accepted value of C_1 is $0.10\mu\text{F}$.

$$\text{Slope} = \underline{3.8361} \quad \text{Enter your result to 4 numbers after the decimal point.}$$

$$C_1 = \underline{0.1097} \mu\text{F} \quad (\text{4 numbers after the decimal point.})$$

$$\% \text{ error} = \underline{5.49} \quad (\text{2 numbers after the decimal point.})$$

- (3) Enter your value of the half time (**2 numbers after the decimal point**) for the parallel and the series capacitor connects, and use these values to calculate C_{parallel} and C_{series} . **Enter your results for capacitors to 3 numbers after the decimal point, and show your calculations on the back of this page.**

$$t_{\text{parallel}} = \underline{4.900} \text{ msec} \quad t_{\text{series}} = \underline{1.224} \text{ msec}$$

$$C_{\text{parallel}} = \underline{.202} \mu\text{F} \quad C_{\text{series}} = \underline{.051} \mu\text{F}$$

- (4) Can the resistance of the function generator be ignored in this experiment? Use 5% as a limit for this problem.

$$\text{Here, } \% \text{ error} = (|R - R_1| / |R_1|) * 100\% \quad \text{or, } \% \text{ error} = (|R_g / R_1|) * 100\%$$

$$\% \text{ error} = \underline{.14\%} \quad (\text{2 numbers after the decimal point.})$$

Circle ☒ **Yes** or No

- (5) Use your experimental values of C_1 and C_{series} to calculate C_2 . **Enter your result to 3 numbers after the decimal point, and show your calculations.**

$$C_2 = \underline{.098} \mu\text{F} \quad (\text{3 numbers after the decimal point.})$$