

## Capacitor Series and Parallel Quick Sheet

Print Last Name \_\_\_\_\_ Print First Name \_\_\_\_\_

Section \_\_\_\_\_ Date \_\_\_\_\_ TA \_\_\_\_\_

Lab Partner \_\_\_\_\_

- (1) **Measured values** of  $R_1$ ,  $C_1$  and  $C_2$ .  $C_1$  is already connected to  $R_1$ . Use the  $1\mu\text{F}$  range on the multimeter when measuring capacitance.

$$R_1 = \text{_____} \quad R_g = \text{_____} \quad R = R_1 + R_g = \text{_____}$$

$$C_1 = \text{_____} \quad C_2 = \text{_____} \quad (\text{Three numbers after the decimal point.})$$

- (2) Using the slope from Excel and equation 9, calculate the capacitance of the first capacitor  $C_1$ . Calculate the % error, where the accepted value of  $C_1$  is  $0.10\mu\text{F}$ .

$$\text{Slope} = \text{_____} \quad \text{Enter your result to 4 numbers after the decimal point.}$$

$$C_1 = \text{_____} \mu\text{F} \quad (\text{4 numbers after the decimal point.})$$

$$\% \text{ error} = \text{_____} \quad (\text{2 numbers after the decimal point.})$$

- (3) Enter your value of the half time (**2 numbers after the decimal point**) for the parallel and the series capacitor connects, and use these values to calculate  $C_{\text{parallel}}$  and  $C_{\text{series}}$ . **Enter your results for capacitors to 3 numbers after the decimal point, and show your calculations on the back of this page.**

$$t_{\text{parallel}} = \text{_____} \text{ msec} \quad t_{\text{series}} = \text{_____} \text{ msec}$$

$$C_{\text{parallel}} = \text{_____} \mu\text{F} \quad C_{\text{series}} = \text{_____} \mu\text{F}$$

- (4) Can the resistance of the function generator be ignored in this experiment? Use 5% as a limit for this problem.

$$\text{Here, } \% \text{ error} = (|R - R_1| / |R_1|) * 100\% \quad \text{or, } \% \text{ error} = (|R_g / R_1|) * 100\%$$

$$\% \text{ error} = \text{_____} \quad (\text{2 numbers after the decimal point.})$$

Circle **Yes** or **No**

- (5) Use your experimental values of  $C_1$  and  $C_{\text{series}}$  to calculate  $C_2$ . **Enter your result to 3 numbers after the decimal point, and show your calculations.**

$$C_2 = \text{_____} \mu\text{F} \quad (\text{3 numbers after the decimal point.})$$