

Resonance Quick Sheet

Print Last Name _____ Print First Name _____

Section _____ Date _____ TA _____

(1) **Values:**

C_1 (μF) = _____ C_2 (μF) = _____

(2) Measurement with one capacitor.

C_1 (F) = _____ **Enter your result in scientific notation.**

f_0 = _____ **Enter your result to 4 digits.**

(3) Measurement with capacitors in series.

C_{series} (F) = _____ **Enter your result in scientific notation.**

f_0 = _____ **Enter your result to 4 digits.**

(4) Measurement with capacitors in parallel.

C_{parallel} (F) = _____ **Enter your result in scientific notation.**

f_0 = _____ **Enter your result to 4 digits.**

(5) Results.

L_{exp} (mH) = _____

% difference = _____