

Kirchhoff's Law Quick Sheet

Print Last Name _____ Print First Name _____

Section _____ Date _____ TA _____

Lab Partner _____

(1) **Individual Resistors Measured (34405A)** $R_1 =$ _____ $R_2 =$ _____ $R_3 =$ _____

(2) **Parallel Combination Measured (34405A)** **Experimental:** $R_p =$ _____

Theoretical: $R_p = [1/R_1 + 1/R_2 + 1/R_3]^{-1} =$ _____ (use measured values of R)

Series Combination Measured (34405A) **Experimental:** $R_s =$ _____

Theoretical: $R_s = R_1 + R_2 + R_3 =$ _____ (use measured values of R)

(3) **Study of Simple Circuits: Kirchhoff's Voltage Law**

Applied Voltage $V_{emf} =$ _____ (Ten Volts) **Part 3B Experimental:** $I =$ _____

Measured (Agilent 34405A)

All values should be positive.

$V_1 =$ _____

$V_2 =$ _____

$V_3 =$ _____

Predicted $V = IR$ (Use I Experimental & R Measured)

All values should be positive.

$V_1 =$ _____

$V_2 =$ _____

$V_3 =$ _____

Verification of Kirchhoff's Law $V_{emf} = V_1 + V_2 + V_3$

Using Measured values: $V_{emf} =$ _____ Using Predicted values: $V_{emf} =$ _____

(4) **Study of Simple Circuits: Kirchhoff's Current Law**

Applied Voltage = _____ (Five Volts)

Individual Measured Voltages and Currents. The node will be the low potential for measurements.

(Measured results will be both positive and negative.)

$I_1 =$ _____ $V_1 =$ _____

$I_2 =$ _____ $V_2 =$ _____

$I_3 =$ _____ $V_3 =$ _____

Predicted Currents (Use voltages measured in **Part (4)**, and the above **Part (1)** resistor measurements.)

$I_1^* =$ _____ $I_2^* =$ _____ $I_3^* =$ _____

Verification of Kirchhoff's Current Law $I_1 + I_2 + I_3 = 0$

Using Measured values from Part 4B: $I_1 + I_2 + I_3 =$ _____

Using Predicted Values from Part 4C: $I_1^* + I_2^* + I_3^* =$ _____